

LRC Circuits and Working of Radio

A Comprehensive Analysis of Theory and Applications

Team Members:

B23136 Jivansh Malik
B23171 Preetam Kumar
B23114 Aman Biswal
B23113 Alok Kumar Prajapati
B23126 Dipanshu
B23116 Anand Pratap Singh
B24274 Ravindra Kumar

April 22, 2025

Contents

1	Introduction	2
2	Theory of LRC Circuits	3
2.1	Components and Basic Principles	3
2.2	Mathematical Description	3
2.3	Resonance Phenomenon	4
2.4	Q Factor	5
3	Radio Technology Fundamentals	6
3.1	Electromagnetic Waves and Radio Spectrum	6
3.2	Radio Transmitters	6
3.3	Modulation Techniques	7
3.4	Radio Receivers	8
4	Implementation in Software	9
4.1	Simulation Environment Setup	9
4.2	Series LRC Circuit Simulation	9
4.3	Frequency Response Analysis	11
4.4	AM Radio Simulation	12
4.5	Interactive Tuning Circuit	14
5	Practical Applications	15
5.1	AM/FM Radio Receivers	15
5.2	Wireless Communication Systems	15
5.3	Emerging Technologies	16
6	Conclusion	17
7	Roles and Responsibilities	18
8	Acknowledgements	19

1. Introduction

Electrical oscillations form the foundation of modern communication systems, with LRC circuits being one of the most fundamental building blocks in radio technology. An LRC circuit comprised of an inductor (L), a resistor (R), and a capacitor (C) exhibits fascinating behavior that enables the generation, transmission, and reception of electromagnetic waves. These components, when arranged in specific configurations, can create oscillations that form the basis of radio communication.

Radio technology has transformed human civilization since its development in the late 19th century. From Marconi's first transatlantic transmission in 1901 to today's sophisticated digital radio systems, the fundamental principles have remained remarkably consistent while the implementations have evolved dramatically. At its core, radio technology allows information to be transmitted through space without physical connections, enabling everything from broadcast entertainment to critical emergency communications.

The physics underlying radio technology involves the interconversion of energy between electric and magnetic fields. In an LRC circuit, energy oscillates between the magnetic field of the inductor and the electric field of the capacitor, with the resistor dissipating some energy during each cycle. This oscillatory behavior, when properly controlled, can be used to create, modulate, and detect radio frequency signals.

This report explores the intricate relationship between LRC circuits and radio technology, examining both theoretical foundations and practical applications. We will investigate the mathematical descriptions of these systems, simulate their behavior using computational tools, and explore how the principles apply in real-world radio systems. Through this exploration, we aim to demonstrate how fundamental physical principles manifest in technology that has become ubiquitous in modern society.

Understanding these principles is not merely of academic interest; it provides insight into the technologies that enable wireless communication in countless devices, from traditional AM/FM radios to smartphones, satellite communications, and emerging technologies like software-defined radio. As we progress through this report, we will bridge the gap between theoretical physics and practical engineering, showing how abstract differential equations translate into devices that have revolutionized human communication.

2. Theory of LRC Circuits

2.1 Components and Basic Principles

The three fundamental components of an LRC circuit each play a distinct role in the system's behavior:

- **Inductor (L):** Stores energy in a magnetic field when current flows through it. Inductors resist changes in current according to Faraday's law of induction. The voltage across an inductor is proportional to the rate of change of current: $V_L = L \frac{dI}{dt}$
- **Resistor (R):** Dissipates energy as heat. The voltage across a resistor is proportional to the current flowing through it, according to Ohm's law: $V_R = IR$
- **Capacitor (C):** Stores energy in an electric field between its plates. Capacitors resist changes in voltage, and the current through a capacitor is proportional to the rate of change of voltage: $I_C = C \frac{dV}{dt}$

When these components are connected in a circuit, they create a system that can oscillate at specific frequencies. This property forms the foundation of radio technology.

2.2 Mathematical Description

The behavior of an LRC circuit can be described by a second-order differential equation. For a series LRC circuit, applying Kirchhoff's voltage law gives:

$$L \frac{d^2 Q}{dt^2} + R \frac{dQ}{dt} + \frac{1}{C} Q = V(t) \quad (2.1)$$

Where:

- Q is the charge on the capacitor
- $V(t)$ is any external voltage source

For a parallel LRC circuit, the governing equation becomes:

$$\frac{d^2 V}{dt^2} + \frac{1}{RC} \frac{dV}{dt} + \frac{1}{LC} V = \frac{1}{LC} V_{in}(t) \quad (2.2)$$

Where V is the voltage across all three components.

These equations are analogous to the equation of a damped harmonic oscillator in mechanical systems. The solution to these equations depends on the relative values of L , R , and C , leading to three possible scenarios:

1. **Underdamped:** When $R < 2\sqrt{\frac{L}{C}}$, the circuit oscillates with decreasing amplitude.
2. **Critically damped:** When $R = 2\sqrt{\frac{L}{C}}$, the circuit returns to equilibrium in minimum time without oscillating.
3. **Overdamped:** When $R > 2\sqrt{\frac{L}{C}}$, the circuit returns to equilibrium without oscillation, but more slowly than the critically damped case.

For radio applications, the underdamped scenario is most relevant, as it allows for oscillations.

2.3 Resonance Phenomenon

The most critical property of LRC circuits for radio applications is resonance. At a specific frequency, known as the resonant frequency, the inductive reactance and capacitive reactance become equal in magnitude but opposite in phase, effectively canceling each other out.

The resonant frequency of a series or parallel LRC circuit is given by:

$$f_0 = \frac{1}{2\pi\sqrt{LC}} \quad (2.3)$$

At resonance, several important phenomena occur:

- In a series LRC circuit, impedance is minimized, resulting in maximum current
- In a parallel LRC circuit, impedance is maximized, resulting in minimum current
- The circuit exhibits a peak response to driving frequencies near resonance

- Energy transfer between the electric field (capacitor) and magnetic field (inductor) is maximized

This selective frequency response is crucial for radio applications, allowing circuits to be tuned to specific frequencies while rejecting others.

2.4 Q Factor

The quality factor (Q factor) of an LRC circuit measures how underdamped the circuit is, or equivalently, how narrow its resonance peak is:

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}} = \frac{\omega_0 L}{R} = \frac{1}{\omega_0 RC} \quad (2.4)$$

A higher Q factor indicates:

- Sharper resonance peak
- Lower energy loss per cycle
- Ability to select a narrower band of frequencies
- Higher sensitivity in radio receivers
- Better frequency stability in radio transmitters

The bandwidth of an LRC circuit is related to the Q factor by:

$$BW = \frac{f_0}{Q} \quad (2.5)$$

This relationship demonstrates why high-Q circuits are desirable for selective radio frequency applications.

3. Radio Technology Fundamentals

3.1 Electromagnetic Waves and Radio Spectrum

Radio technology fundamentally relies on the generation, transmission, and reception of electromagnetic waves. These waves, first predicted by James Clerk Maxwell and experimentally confirmed by Heinrich Hertz, consist of coupled electric and magnetic fields that propagate through space at the speed of light.

The radio frequency spectrum ranges from about 3 kHz to 300 GHz, divided into bands:

- Very Low Frequency (VLF): 3-30 kHz
- Low Frequency (LF): 30-300 kHz
- Medium Frequency (MF): 300 kHz-3 MHz (includes AM broadcasting)
- High Frequency (HF): 3-30 MHz
- Very High Frequency (VHF): 30-300 MHz (includes FM broadcasting)
- Ultra High Frequency (UHF): 300 MHz-3 GHz
- Super High Frequency (SHF): 3-30 GHz
- Extremely High Frequency (EHF): 30-300 GHz

Each band has distinct propagation characteristics that make it suitable for different applications.

3.2 Radio Transmitters

A basic radio transmitter consists of several key components:

1. **Oscillator:** Typically an LRC circuit that generates the carrier frequency
2. **Modulator:** Impresses information onto the carrier wave

3. **Power amplifier:** Increases the signal strength
4. **Antenna:** Converts electrical signals into electromagnetic waves

The oscillator circuit is where LRC principles are most directly applied. By carefully selecting the values of L, C, and R, the circuit can be designed to oscillate at a specific frequency. Common oscillator circuits include:

- **Hartley oscillator:** Uses a tapped inductor
- **Colpitts oscillator:** Uses a tapped capacitor
- **Armstrong oscillator:** Uses transformer coupling
- **Crystal oscillator:** Uses a piezoelectric crystal for greater frequency stability

3.3 Modulation Techniques

To transmit information, the carrier wave must be modulated. The three primary modulation methods are:

1. **Amplitude Modulation (AM):**

The amplitude of the carrier wave is varied according to the information signal. Mathematically represented as:

$$v(t) = A_c[1 + m \sin(\omega_m t)] \sin(\omega_c t) \quad (3.1)$$

Where:

- A_c is the carrier amplitude
- m is the modulation index
- ω_m is the modulating frequency
- ω_c is the carrier frequency

2. **Frequency Modulation (FM):**

The frequency of the carrier wave is varied according to the information signal. Mathematically represented as:

$$v(t) = A_c \sin[\omega_c t + \beta \sin(\omega_m t)] \quad (3.2)$$

Where β is the modulation index for FM.

3. Phase Modulation (PM):

The phase of the carrier wave is varied according to the information signal.

In all these modulation techniques, LRC circuits play crucial roles in generating, modifying, and filtering the signals.

3.4 Radio Receivers

Radio receivers perform the inverse operation of transmitters, extracting the original information signal from the modulated carrier wave. The key components include:

1. **Antenna:** Captures electromagnetic waves and converts them to electrical signals
2. **Tuner:** Selects the desired frequency (typically using an LRC circuit)
3. **Detector/Demodulator:** Extracts the information signal from the modulated carrier
4. **Amplifier:** Strengthens the signal
5. **Output device:** Converts electrical signals to sound or other useful forms

The most important application of LRC circuits in receivers is in the tuning circuit. By adjusting either the inductor or (more commonly) the capacitor, the resonant frequency can be changed, allowing the receiver to select different stations.

Two common receiver architectures are:

- **Superheterodyne receiver:** Uses frequency mixing to convert the received signal to an intermediate frequency for easier processing
- **Direct conversion receiver:** Converts the RF signal directly to baseband

4. Implementation in Software

4.1 Simulation Environment Setup

For our implementation, we utilized Python along with the SciPy, NumPy, and Matplotlib libraries, chosen for their robust numerical computation capabilities and effective data visualization tools.

The complete simulation code can be accessed in our GitHub repository: [<https://github.com/dipanshu849/Waves-Report.git>].

4.2 Series LRC Circuit Simulation

To simulate a series LRC circuit, we implemented the differential equation:

$$L \frac{d^2 I}{dt^2} + R \frac{dI}{dt} + \frac{1}{C} I = \frac{dV_{in}}{dt} \quad (4.1)$$

The function defining this system is:

```
1 def series_lrc_system(t, y, L, R, C, V_func):
2     dydt = np.zeros(2)
3     dydt[0] = y[1] # dI/dt = y[1]
4     dydt[1] = (V_func(t) - R * y[1] - (1/C) * y[0]) / L
5     return dydt
```

For a step voltage input:

```
1 def step_voltage(t, V0=1.0, t0=0):
2     return V0 if t >= t0 else 0
```

We then solved this system for different combinations of L, R, and C values to demonstrate the three damping cases:

```
1 L = 1.0 # in henries
2 C = 1.0 # in farads
3
4 R_under = 0.5 # Underdamped (R < 2*sqrt(L/C))
```

```

5 R_crit = 2.0    # Critically damped (R = 2*sqrt(L/C))
6 R_over = 4.0    # Overdamped (R > 2*sqrt(L/C))
7
8 t_span = (0, 20)
9 t_eval = np.linspace(*t_span, 1000)
10 initial_conditions = [0, 0]
11
12 results_under = solve_ivp(
13     lambda t, y: series_lrc_system(t, y, L, R_under, C, lambda t:
14         step_voltage(t, 1.0)),
15     t_span, initial_conditions, t_eval=t_eval, method='RK45')
16
17 results_crit = solve_ivp(
18     lambda t, y: series_lrc_system(t, y, L, R_crit, C, lambda t:
19         step_voltage(t, 1.0)),
20     t_span, initial_conditions, t_eval=t_eval, method='RK45')
21
22 results_over = solve_ivp(
23     lambda t, y: series_lrc_system(t, y, L, R_over, C, lambda t:
24         step_voltage(t, 1.0)),
25     t_span, initial_conditions, t_eval=t_eval, method='RK45')

```

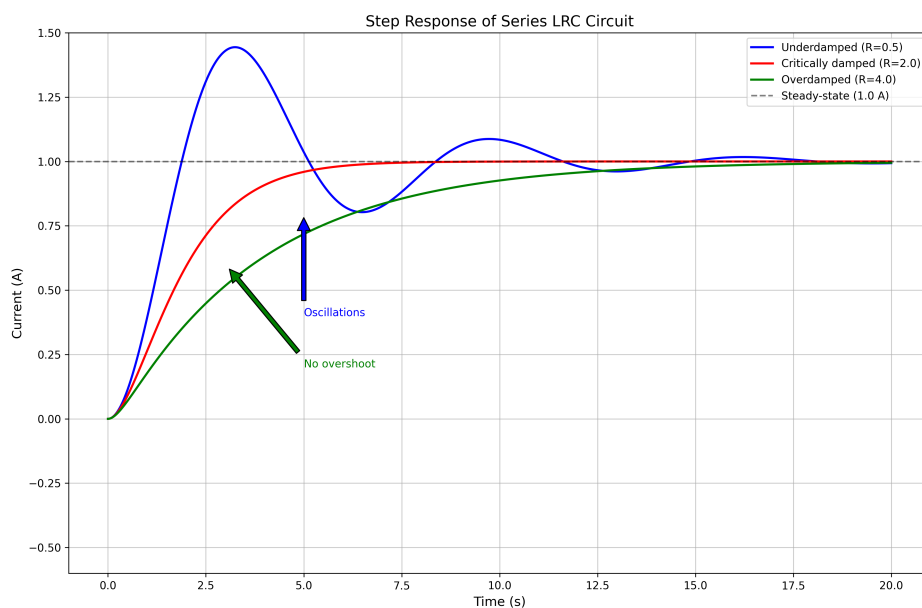


Figure 4.1: Step response of series LRC circuit showing underdamped, critically damped, and overdamped cases.

The results clearly show the different behavior patterns depending on the damping scenario:

1. Underdamped: oscillatory current with decaying amplitude

2. Critically damped: fastest return to steady state without oscillation
3. Overdamped: slower return to steady state without oscillation

4.3 Frequency Response Analysis

To analyze how LRC circuits respond to different frequencies, we implemented a frequency sweep simulation:

```
1 def calculate_frequency_response(L, R, C, freq_range):
2     Z = []
3     for f in freq_range:
4         omega = 2 * np.pi * f
5         Z_L = 1j * omega * L           # Inductor impedance
6         Z_C = 1 / (1j * omega * C)     # Capacitor impedance
7         Z_total = R + Z_L + Z_C        # Total series impedance
8         Z.append(abs(Z_total))         # Magnitude of impedance
9
10    return np.array(Z)
11
12 L = 1.0 # in henries
13 C = 1.0 # in farads
14
15 R_under = 0.5 # Low R gives sharp resonance peak
16 R_crit = 2.0 # Medium R
17 R_over = 4.0 # High R flattens the response
18
19 # (logarithmic scale to better show resonance)
20 freq_range = np.logspace(-1, 1, 1000) # 0.1 Hz to 10 Hz
21
22 f_resonant = 1 / (2 * np.pi * np.sqrt(L * C))
23
24 Z_under = calculate_frequency_response(L, R_under, C, freq_range)
25 Z_crit = calculate_frequency_response(L, R_crit, C, freq_range)
26 Z_over = calculate_frequency_response(L, R_over, C, freq_range)
```

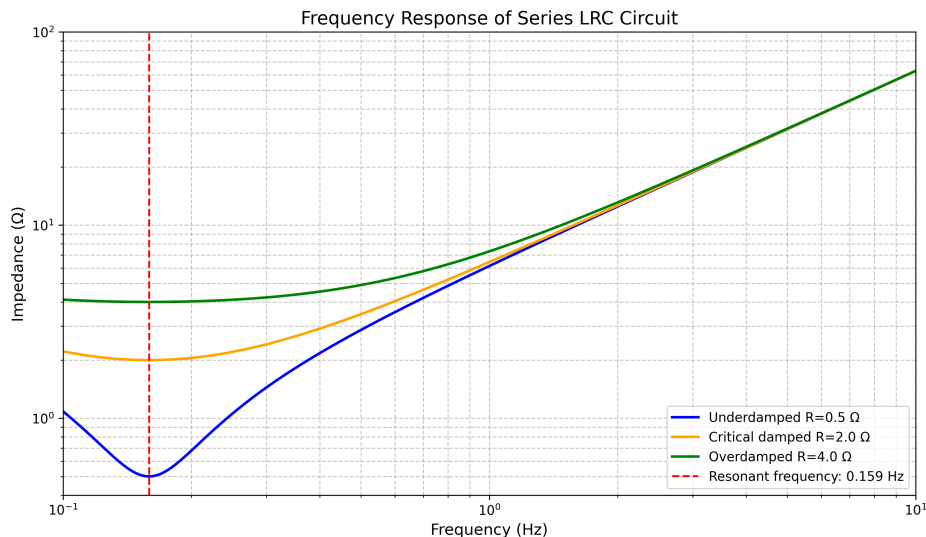


Figure 4.2: Frequency response of series LRC circuit showing impedance magnitude versus frequency for different damping scenarios, with the resonant frequency highlighted.

The frequency response plots clearly demonstrate the resonance phenomenon, with a sharp impedance minimum at the resonant frequency for the underdamped case. This selective frequency response is what allows radio tuners to isolate specific broadcast channels.

4.4 AM Radio Simulation

To simulate AM radio transmission and reception, we implemented modulation and demodulation functions:

```

1 def generate_message_signal(t, freq=0.1):
2     # (e.g., an audio tone)
3     return np.sin(2 * np.pi * freq * t)
4
5 def am_modulate(message, carrier_freq, t, modulation_index=0.5):
6     carrier = np.sin(2 * np.pi * carrier_freq * t)
7     return (1 + modulation_index * message) * carrier
8
9 def envelope_detector_improved(modulated_signal):
10    # Using Hilbert transform
11
12    analytic_signal = hilbert(modulated_signal)
13    envelope = np.abs(analytic_signal)
14    # (approximation)
15    envelope = envelope - np.mean(envelope)
16    # Scale to match original amplitude

```

```

17     scaling_factor = np.max(np.abs(modulated_signal)) / np.max(np.abs(
    (envelope))
18     return envelope * scaling_factor

```

We then simulated the complete AM radio process:

```

1 t = np.linspace(0, 1, 50000)
2 message_freq = 5      # Hz
3 carrier_freq = 100    # Hz
4
5 message = generate_message_signal(t, message_freq)
6 modulated = am_modulate(message, carrier_freq, t, modulation_index
    =0.8)
7
8 demodulated = envelope_detector_improved(modulated)

```

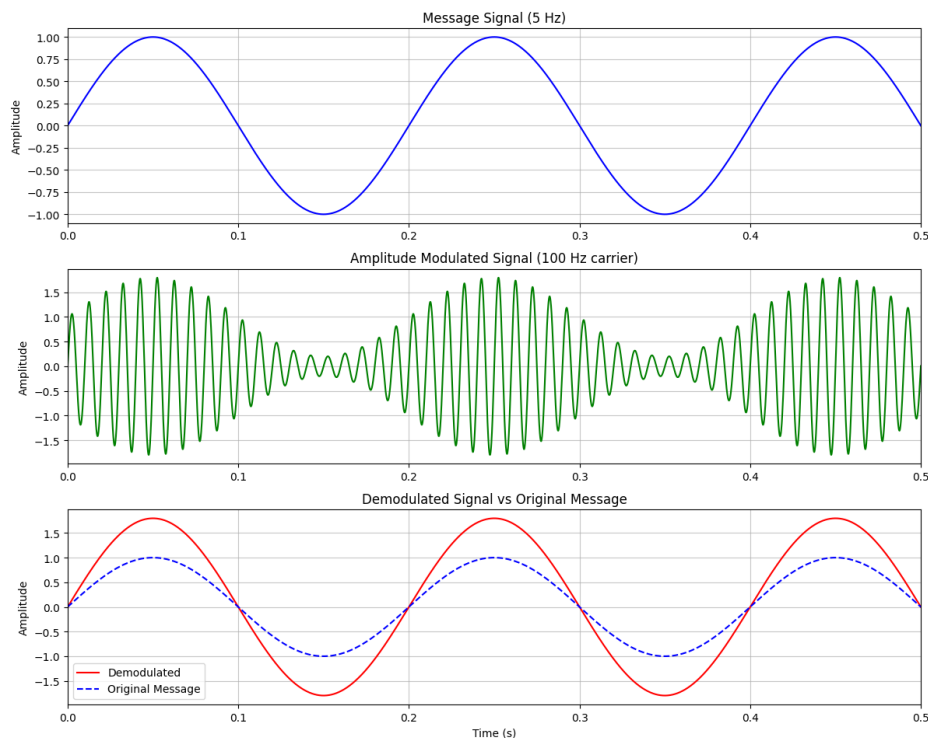


Figure 4.3: AM radio simulation showing the original message signal (top), modulated signal (middle), and demodulated signal compared to the original (bottom).

The simulation demonstrates how information (the message signal) can be transmitted via radio waves using amplitude modulation, and then recovered using an envelope detector.

4.5 Interactive Tuning Circuit

To demonstrate how varying the capacitance in an LRC circuit allows for tuning to different radio frequencies, we created an interactive simulation:

```

1
2 def calculate_frequency_response(L, R, C, freq_range):
3     Z = []
4     for f in freq_range:
5         omega = 2 * np.pi * f
6         Z_L = 1j * omega * L           # Inductor impedance
7         Z_C = 1 / (1j * omega * C)     # Capacitor impedance
8         Z_total = R + Z_L + Z_C        # Total series impedance
9         Z.append(abs(Z_total))         # Magnitude of impedance
10
11     return np.array(Z)

```

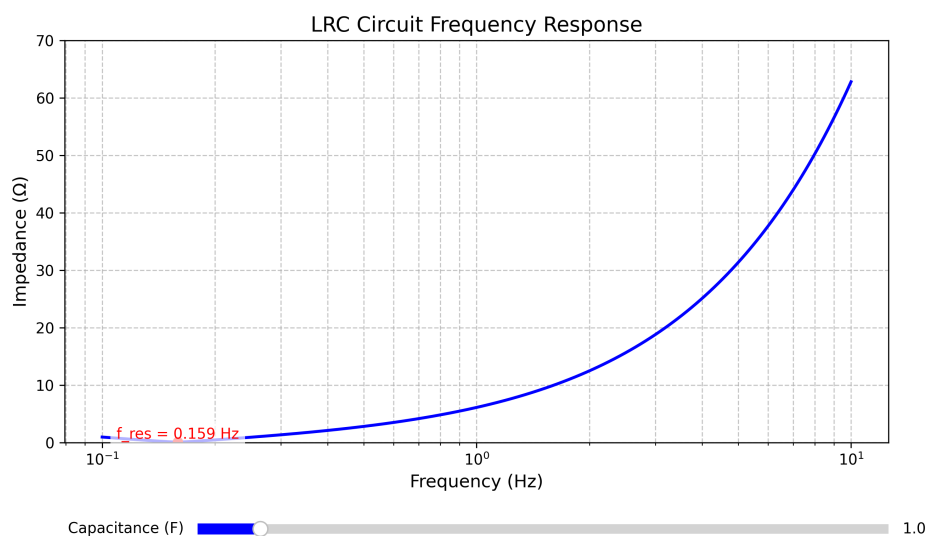


Figure 4.4: Screenshot of the interactive tuning circuit simulation showing how changing capacitance affects the resonant frequency.

This interactive tool allows users to see how changing the capacitance changes the resonant frequency of the circuit, demonstrating the principle behind tuning dials on traditional radio receivers.

5. Practical Applications

5.1 AM/FM Radio Receivers

The principles of LRC circuits are directly applied in radio receivers, where they serve several crucial functions:

1. **RF Tuning:** The front-end tuning circuit uses a variable capacitor in conjunction with an inductor to select a particular radio station frequency. By varying the capacitance, the resonant frequency changes, allowing different stations to be received.
2. **Intermediate Frequency (IF) Filters:** In superheterodyne receivers, LRC circuits create bandpass filters at the intermediate frequency (typically 455 kHz for AM, 10.7 MHz for FM). These filters improve selectivity, allowing the receiver to separate closely spaced stations.
3. **Local Oscillators:** LRC-based oscillator circuits generate the frequencies needed for superheterodyne mixing.
4. **Demodulation:** In AM receivers, LC circuits can be part of the envelope detector system. In FM receivers, they are used in discriminator circuits for demodulation.

Modern digital radios still utilize these principles, though often implemented using integrated circuits rather than discrete components.

5.2 Wireless Communication Systems

Beyond traditional radio broadcasting, the principles of the LRC circuit extend to numerous wireless communication systems.

1. **Mobile Phones:** RF filters and oscillators in cellular devices use LRC principles, although often implemented using surface acoustic wave (SAW) filters and crystal oscillators for better performance.

2. **Wi-Fi and Bluetooth:** These technologies operate at microwave frequencies (2.4 GHz, 5 GHz) but still rely on resonant circuits for frequency selection, though implemented as microstrip or integrated circuits.
3. **GPS Receivers:** Precise frequency selection is critical for receiving satellite navigation signals, again employing resonance principles.
4. **RFID Systems:** Both passive and active RFID tags use LC resonant circuits to capture energy and transmit data.

5.3 Emerging Technologies

New applications continue to emerge, including:

1. **Software-Defined Radio (SDR):** Digital systems that implement traditional radio functions in software but still require front-end LRC circuits for initial filtering and amplification.
2. **Wireless Power Transfer:** Uses resonant coupling between LC circuits to transfer energy without wires.
3. **Ultra-Wideband (UWB) Communication:** Uses extremely short pulses rather than continuous waves, but still requires precision timing circuits based on LC oscillators.
4. **Internet of Things (IoT) devices:** Low-power communication modules often use simple resonant circuits to minimize energy consumption.

Through these diverse applications, the fundamental principles of LRC circuits continue to shape modern communication technologies, demonstrating the enduring relevance of these basic electronic components.

6. Conclusion

Our exploration of LRC circuits and their application in radio technology has demonstrated the elegant connection between theoretical physics and practical engineering.

The key findings of our study include:

1. LRC circuits exhibit resonance phenomena that allow them to selectively respond to specific frequencies, forming the foundation for radio frequency tuning and filtering.
2. The Q factor of these circuits critically determines their selectivity and efficiency, with higher Q values enabling a more precise frequency selection.
3. Software simulation provides a powerful tool for understanding and visualizing the behavior of these circuits under various conditions, offering insights that might be challenging to observe in physical experiments.
4. Despite the advent of digital technology, the principles underlying LRC circuits remain fundamental to modern radio and wireless communication systems, from traditional AM/FM broadcasting to cutting-edge software-defined radio and IoT devices.

The ability of these circuits to resonate at specific frequencies enables the selective transmission and reception of electromagnetic waves, allowing information to be wirelessly transmitted across vast distances.

As wireless technology continues to evolve, the fundamental principles of LRC circuits will remain relevant, although often implemented in increasingly miniaturized and integrated forms. Understanding these principles provides a foundation for appreciating both historical developments in radio technology and emerging innovations in wireless communication.

7. Roles and Responsibilities

B23136 Jivansh Malik

- Communication about the project with the instructor.
- Contributed to the presentation of the final presentation.

B23113 Alok Kumar Prajapati

- Contributed to the presentation of the final presentation.
- Reviewed and refined presentation content for clarity and consistency.

B23171 Preetam Kumar

- Designed presentation slides and supporting visual materials.

B23116 Anand Pratap Singh

- Contributed to the creation of presentation slides.

B23114 Aman Biswal

- Authored Report Sections 5 and 6, covering practical applications and conclusions.

B23126 Dipanshu

- Compilation of the report.
- Authored Report Sections 3 and 4, focusing on radio technology and software implementation.

B24274 Ravindra Kumar

- Contributed to Report Sections 1, 2, covering the introduction and theoretical background of LRC circuits.

8. Acknowledgements

We would like to express our sincere gratitude to Dr. Krishna Mohan Parattu for a course that encourages the practical application of theoretical concepts. His insights into oscillator systems have been invaluable in shaping our understanding of the subject.

Our appreciation extends to the open-source community behind the Python scientific computing stack, particularly the developers of NumPy, SciPy, and Matplotlib, whose tools enabled our computational exploration of LRC circuit behavior.

Finally, we thank our peers who provided constructive feedback during informal discussions about this project, helping us refine our approach and presentation.